

Lab 8: Impedance

Jonah Spector

May 3, 2025


1 Introduction


Impedance is an important tool for analyzing AC circuits, especially those with inductors and/or capacitors. In this lab, we learn some basic principles about impedance, including phase shifting and the difference between the impedance of capacitors and inductors.

2 Part 1

Notes: It was easier to measure the phase difference when the 100 ohm resistor was used in place of the 1000 ohm resistor for the capacitor and vice versa for the inductor.

2.1 Problem 1

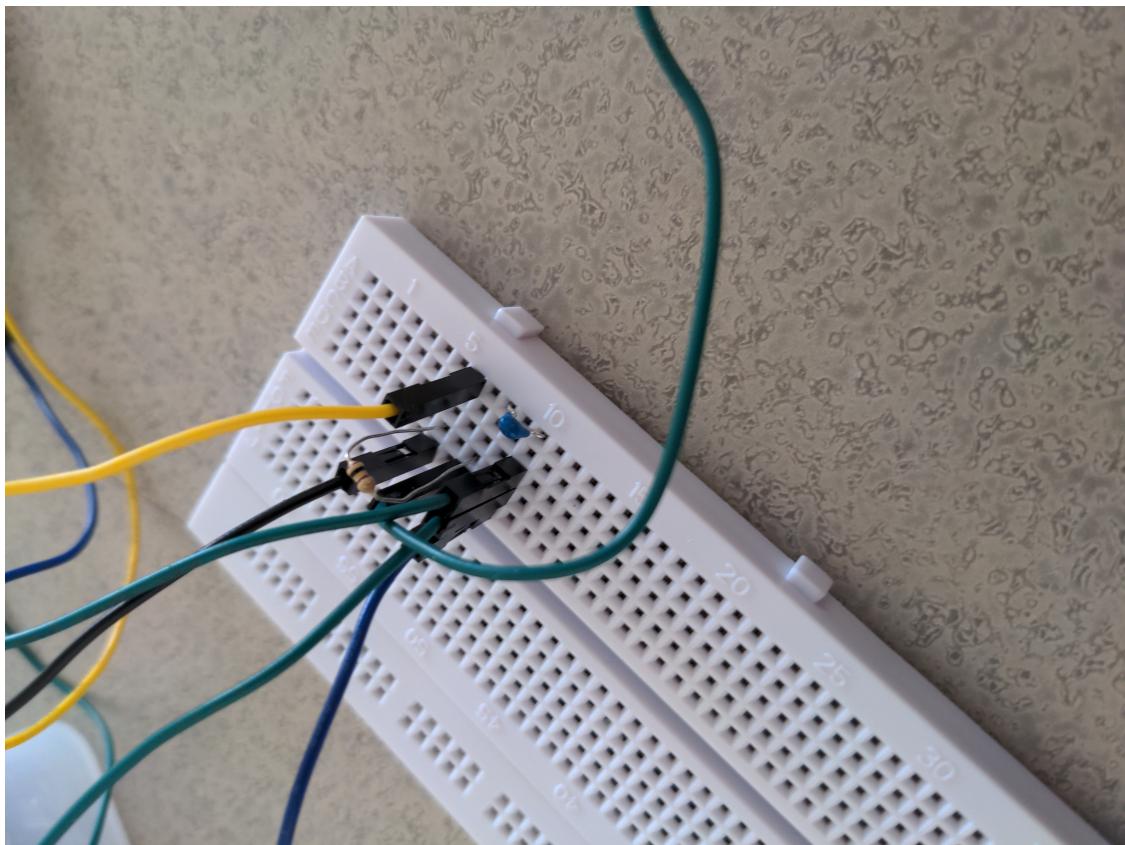

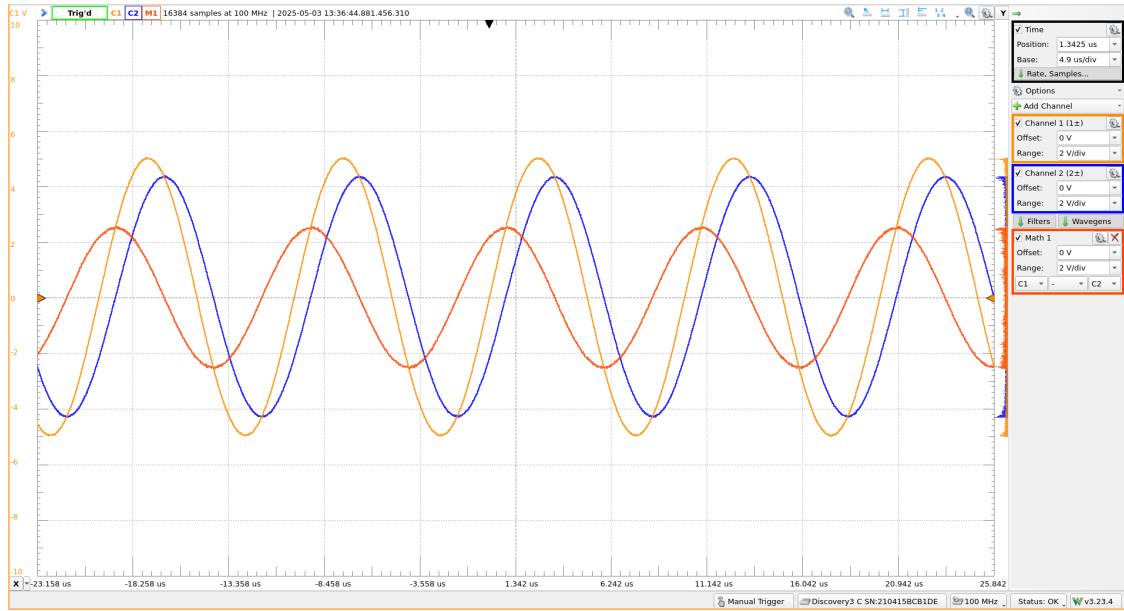

2.2 Problem 2

The table is printed out in Python, so I don't have to have two copies of the data.

```
[33]: from math import *
import matplotlib.pyplot as plt
import numpy as np
from tabulate import tabulate

# Recorded and calculated data

freq = np.array([100, 1e3, 10e3, 100e3, 200e3, 500e3, 1e6, 2e6]) # Hz
v_in = np.array([4.9982, 4.9949, 5.0062, 4.9731, 4.9618, 4.9429, 4.8748, 4.
    ↪9448]) # V
v_c = np.array([4.9949, 4.9968, 5.0359, 4.2939, 3.2303, 1.6595, 0.89385, 0.
    ↪44316]) # V
v_r = np.array([0.0023, 0.0208, 0.2547, 2.4556, 3.6433, 4.2735, 4.8445, 4.
    ↪7784]) # V
i = v_r / 100 # 100 ohms, instead of 1k ohms
z = v_c / i # ohms
period = np.array(
    [10e-3, 1e-3, 100.00e-6, 10.003e-6, 4.9997e-6, 1.9979e-6, 1.0016e-6, 498.
    ↪62e-9])
) # s
delta_t = np.array(
    [
        -1.482e-3,
        -229.011e-6,
```

```

        -24.424e-6,
        -2.378e-6,
        -1.173e-6,
        -418.77e-9,
        -219.09e-9,
        -89.49e-9,
    ]
) # s
phase_diff = 360 * delta_t / period # radians --> degrees

# Make table

headers = [
    "Frequency (Hz)",
    "V_in (V)",
    "V_c (V)",
    "V_R (V)",
    "I (A)",
    "Z (ohm)",
    "Period (s)",
    "Delta-T (s)",
    "Phase Diff. (degrees)",
]
table = zip(freq, v_in, v_c, v_r, i, z, period, delta_t, phase_diff)

print(tabulate(table, headers=headers))

```

	Frequency (Hz)	V_in (V)	V_c (V)	V_R (V)	I (A)	Z (ohm)
Period (s)	Delta-T (s)	Phase Diff. (degrees)				
	100	4.9982	4.9949	0.0023	2.3e-05	217170
0.01	-0.001482			-53.352		
	1000	4.9949	4.9968	0.0208	0.000208	24023.1
0.001	-0.000229011			-82.444		
	10000	5.0062	5.0359	0.2547	0.002547	1977.19
0.0001	-2.4424e-05			-87.9264		
	100000	4.9731	4.2939	2.4556	0.024556	174.862
1.0003e-05	-2.378e-06			-85.5823		
	200000	4.9618	3.2303	3.6433	0.036433	88.6641
4.9997e-06	-1.173e-06			-84.4611		
	500000	4.9429	1.6595	4.2735	0.042735	38.8323
1.9979e-06	-4.1877e-07			-75.4578		
	1e+06	4.8748	0.89385	4.8445	0.048445	18.4508
1.0016e-06	-2.1909e-07			-78.7464		
	2e+06	4.9448	0.44316	4.7784	0.047784	9.27423
4.9862e-07	-8.949e-08			-64.6111		

2.3 Problem 3


```
[34]: fig, (ax1, ax2) = plt.subplots(2)

fig.suptitle("Capacitor Impedance vs Frequency")

ax1.plot(freq, z)
ax1.set_xlabel("Frequency (Hz)")
ax1.set_ylabel("Impedance (ohms)")
ax1.grid()

ax2.loglog(freq, z)
ax2.set_xlabel("Frequency (Hz)")
ax2.set_ylabel("Impedance (ohms)")
ax2.grid()

fig.tight_layout()
```

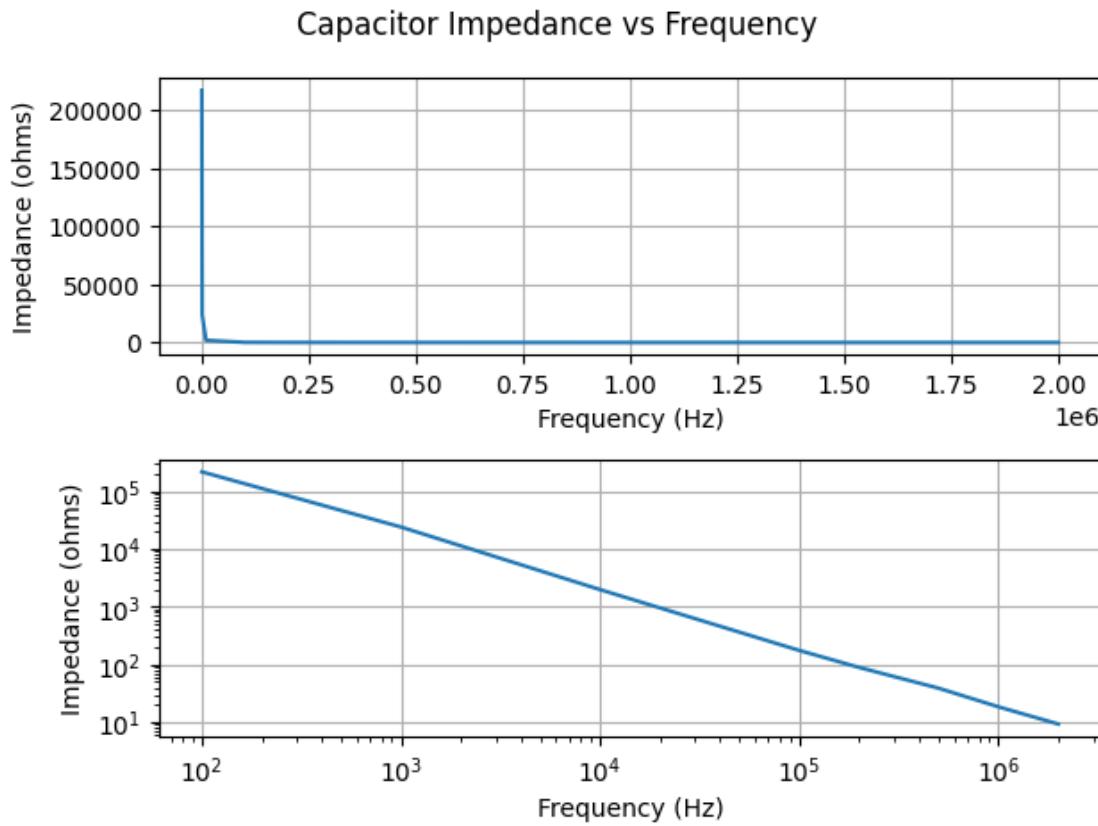

2.4 Problem 4

Since the plot is linear when the variables are both logarithmic, this implies:

$$\log |Z| = m \log f + b$$

$$\log |Z| = \log f^m + b$$

$$b = \log C \implies \log |Z| = \log f^m + \log C$$

$$\log |Z| = \log C f^m \implies |Z| = C f^m = \log(b) f^m$$

$$|Z| = 10^b f^m$$

Using linear regression on the logarithmic data to find m and b :

```
[35]: m, b = np.polyfit(np.log10(freq), np.log10(z), 1)
print(f"\n|Z| = {10**b:4e} * f^{m:4f}")
```

$$|Z| = 2.525705e+07 * f^{-1.023904}$$

The actual equation for the impedance (Wikipedia):

$$Z = -\frac{j}{2\pi f C}$$


The fitted equation matches this perfectly. The constant multiplier in the equation, given a capacitance of 0.01 uF, is: 1.592e7. This is in the same order of magnitude as the fitted constant multiplier.

2.5 Problem 5

The recorded values are in the table. They all agree with the frequency settings.

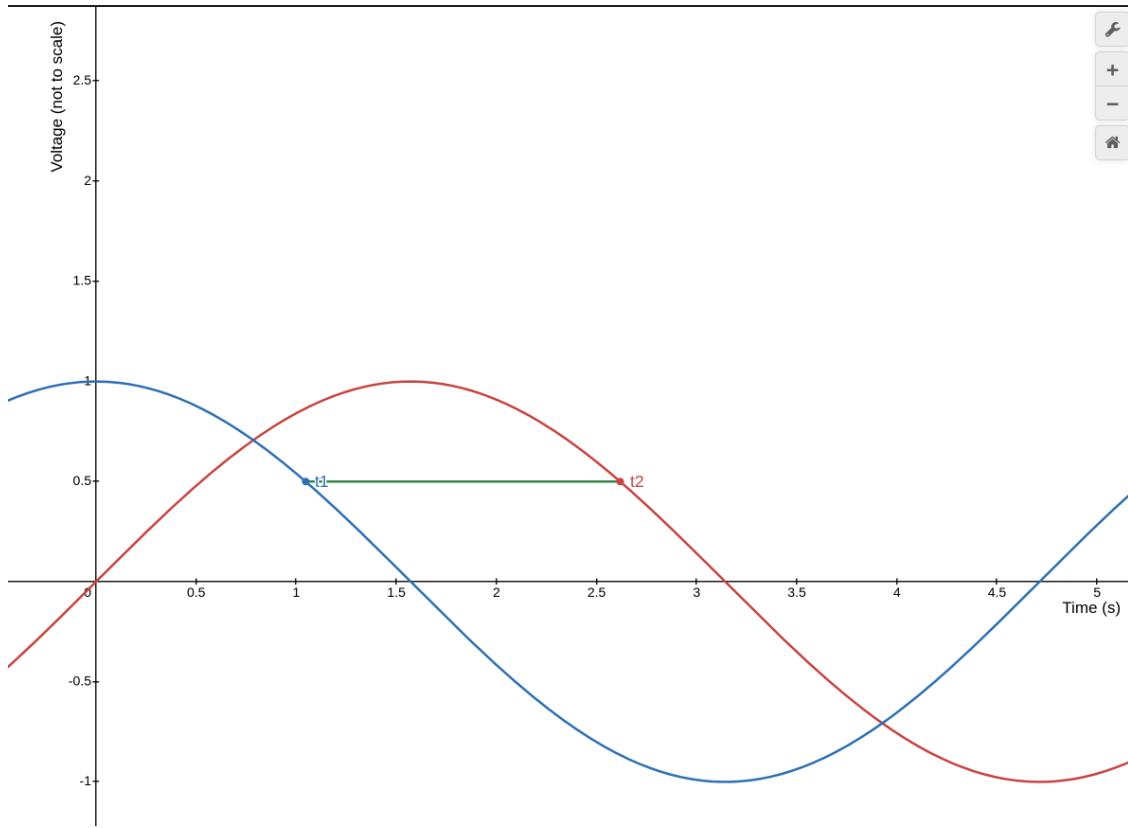2.6 Problem 6

The recorded delta-T values and calculated differences (in degrees) are in the table. Here is a sketch showing phase difference:



The phase difference is simply the length between t_1 and t_2 . The amplitudes of the waves don't matter.

2.7 Problem 7

See table.



2.8 Problem 8

The phase difference seems to be rotating from around 50 degrees, to 90 degrees, and back to 50 degrees. This is a consequence of the imaginary unit in the equation causing the value of the impedance to rotate around the origin.

3 Part 2

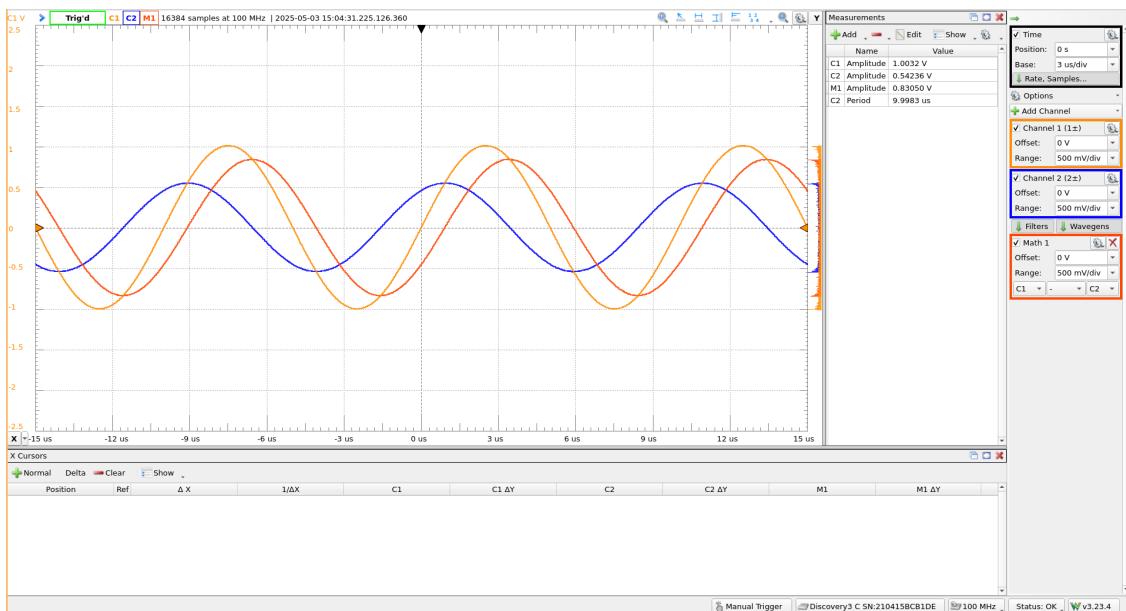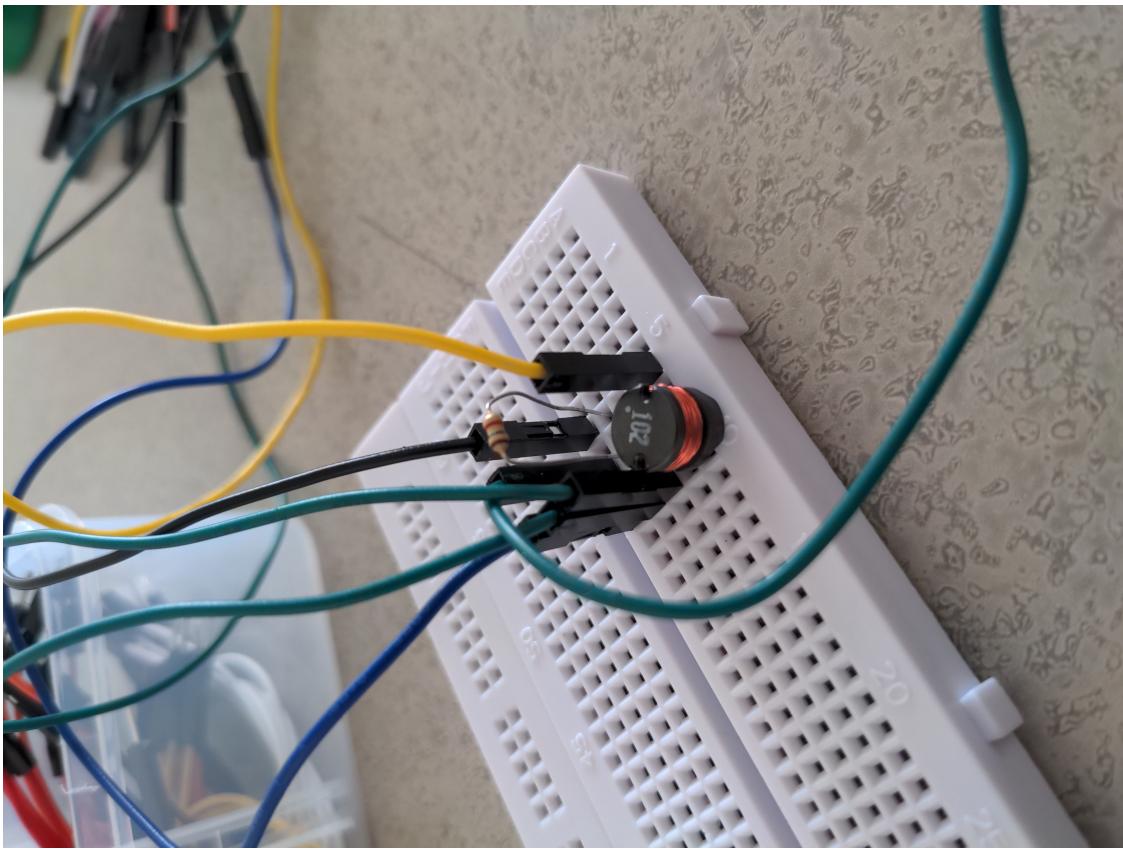3.1 Problem 1

The 1000 ohm resistor is used instead of the 100 ohm resistor.



3.2 Problem 2

```
[36]: # Recorded and calculated data

freq = np.array([100, 1e3, 10e3, 100e3, 200e3, 500e3, 1e6, 2e6]) # Hz
v_in = np.array(
    [0.99828, 0.99939, 1.0021, 1.0037, 1.0024, 1.0032, 0.96045, 0.99312]
) # V
v_l = np.array(
    [2.7184e-3, 6.8784e-3, 62.894e-3, 0.54319, 0.80415, 0.97846, 0.98653, 0.
    ↪88126]
) # V
v_r = np.array(
    [0.99560, 0.99625, 0.99640, 0.83851, 0.58079, 171.17e-3, 92.468e-3, 316.
    ↪43e-3]
) # V
i = v_r / 1000 # 1k ohms, instead of 100 ohms
z = v_l / i # ohms
period = np.array(
    [
        9.9997e-3,
        1.0001e-3,
        100.05e-6,
        10.001e-6,
        5.0002e-6,
        1.9999e-6,
        0.99999e-6,
        0.50008e-6,
    ]
) # s
delta_t = np.array(
    [430e-6, 167.9e-6, 26.45e-6, 4.05e-6, 2.39e-6, -828.4e-9, -338.5e-9, -146.
    ↪0e-9]
) # s
phase_diff = 360 * delta_t / period # radians --> degrees

# Make table

headers = [
    "Frequency (Hz)",
    "V_in (V)",
    "V_L (V)",
    "V_R (V)",
    "I (A)",
    "Z (ohm)",
    "Period (s)",
    "Delta-T (s)",
```

```

    "Phase Diff. (degrees)",
]
table = zip(freq, v_in, v_l, v_r, i, z, period, delta_t, phase_diff)

print(tabulate(table, headers=headers))

```

Frequency (Hz)	V_in (V)	V_L (V)	V_R (V)	I (A)	Z (ohm)
Period (s)	Delta-T (s)	Phase Diff. (degrees)			
100	0.99828	0.0027184	0.9956	0.0009956	2.73041
0.0099997	0.00043		15.4805		
1000	0.99939	0.0068784	0.99625	0.00099625	6.90429
0.0010001	0.0001679		60.438		
10000	1.0021	0.062894	0.9964	0.0009964	63.1212
0.00010005	2.645e-05		95.1724		
100000	1.0037	0.54319	0.83851	0.00083851	647.804
1.0001e-05	4.05e-06		145.785		
200000	1.0024	0.80415	0.58079	0.00058079	1384.58
5.0002e-06	2.39e-06		172.073		
500000	1.0032	0.97846	0.17117	0.00017117	5716.31
1.9999e-06	-8.284e-07		-149.119		
1e+06	0.96045	0.98653	0.092468	9.2468e-05	10668.9
9.9999e-07	-3.385e-07		-121.861		
2e+06	0.99312	0.88126	0.31643	0.00031643	2785.01
5.0008e-07	-1.46e-07		-105.103		

3.3 Problem 3


```
[39]: fig, (ax1, ax2) = plt.subplots(2)

fig.suptitle("Inductor Impedance vs Frequency")

ax1.plot(freq, z)
ax1.set_xlabel("Frequency (Hz)")
ax1.set_ylabel("Impedance (ohms)")
ax1.grid()

ax2.loglog(freq, z)
ax2.set_xlabel("Frequency (Hz)")
ax2.set_ylabel("Impedance (ohms)")
ax2.grid()

fig.tight_layout()
```

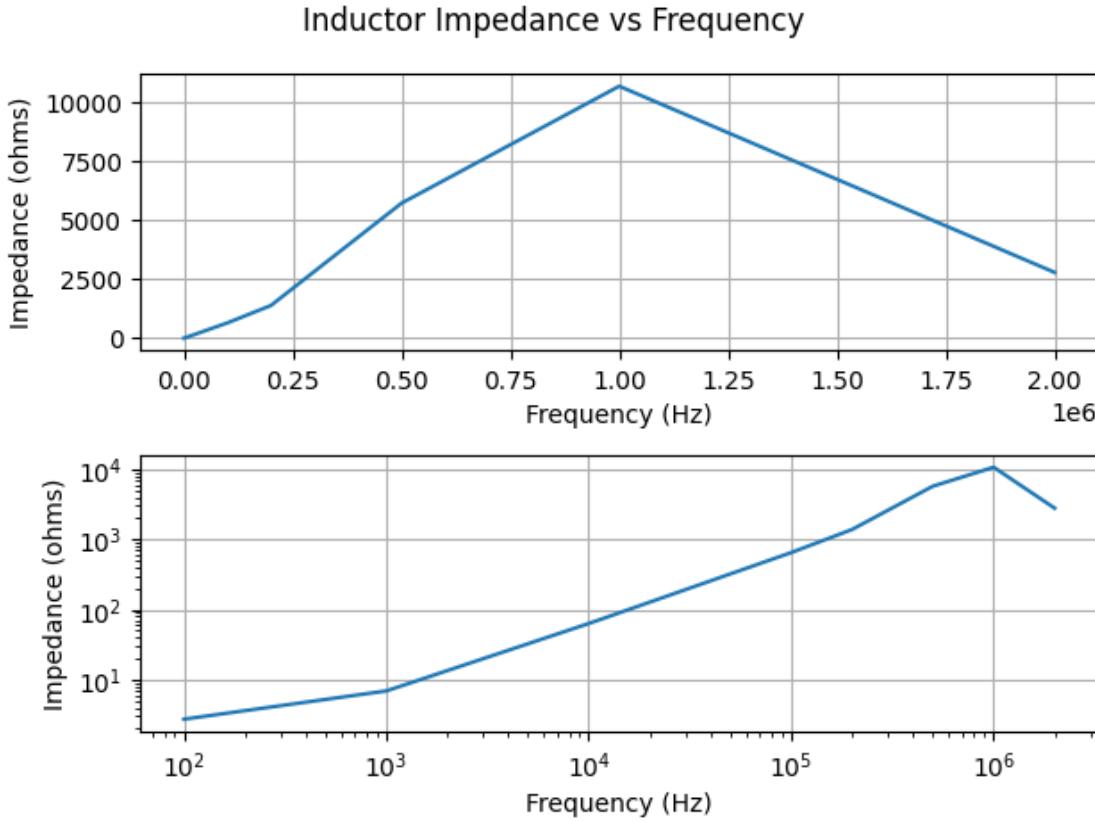

3.4 Problem 4

Using the same math from the previous curve-fitting:

```
[41]: m, b = np.polyfit(np.log10(freq), np.log10(z), 1)
print(f"|Z| = {10**b:.4e} * f^{m:.4f}")
```

$$|Z| = 3.204617 \times 10^{-2} \times f^{0.863572}$$


This is close, but not as close as the capacitor was to its equation, to the actual impedance equation for an inductor:

$$Z = 2\pi f L j$$

The constant multiplier in the fitted equation is off, but the exponent is at least close to being 1.

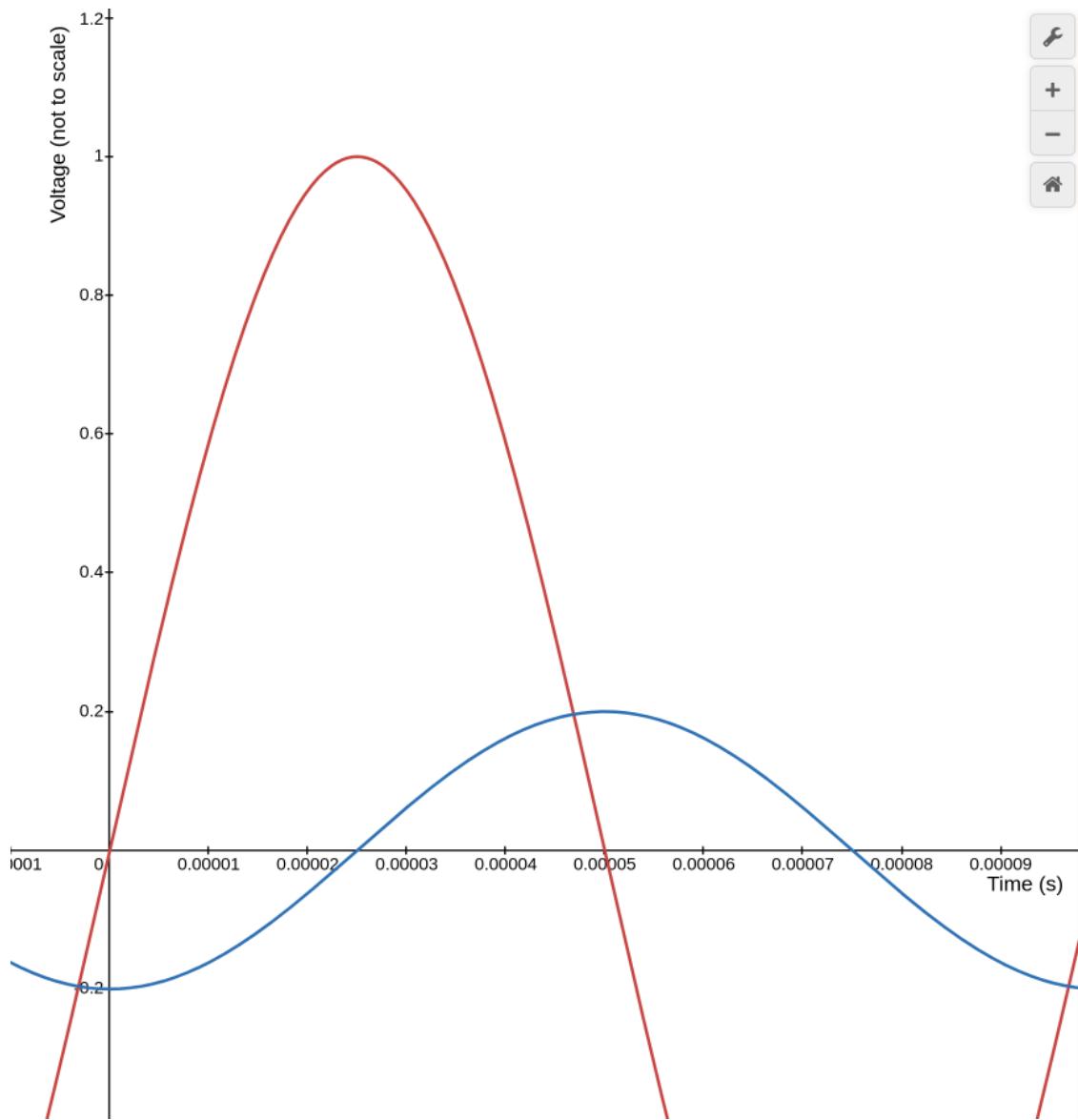3.5 Problem 5

The recorded delta-T values and calculated differences (in degrees) are in the table. Here is a sketch showing phase difference:



3.6 Problem 6

The phase difference rotates up to 180 degrees than flips to -180 around 200 kHz and begins going back to 0 degrees. The inductor's impedance equation doesn't seem to imply a flip in the phase difference, but this is likely due to the internal resistance of the inductor, since it requires a very long wire, or some other factor coming from the fact that a non-ideal inductor was tested.

4 Conclusion

The principles of impedance were all demonstrated here. There were issues measuring the equation for the inductor, but this is likely due to it not being an ideal inductor. The capacitor was much closer to the ideal and was therefore easier to gather data on.