Lab 10 RC Step Response

Jonah Spector

2025 - 05 - 03

Introduction

Understanding the step response of R-C circuits is crucial to understanding more complex circuits and gives insight into the physical properties of capacitors (i.e. what they actually do over time, and not just how they settle into steady-state configurations).

Capacitor and Resistor Calculations

To find a capacitor and resistor value, we start with the step response equation:

$$V(t) = V_{\inf} + [V_0 - V_{\inf}]e^{-\frac{t}{\tau}} \qquad \tau = RC$$

Assuming we start at 0 V and that the maximum voltage is 5 V:

$$V(t) = 5 + [0 - 5]e^{-\frac{t}{RC}}$$

Given the time to reach 50% of 5 V (2.5 V):

$$2.5 = 5 + -5e^{-\frac{10 \times 10^{-6}}{RC}} \implies 1 = 2e^{-\frac{10 \times 10^{-6}}{RC}}$$

$$\ln 1 = \ln \left(2e^{-\frac{10 \times 10^{-6}}{RC}} \right) \implies 0 = \ln 2 - \frac{10 \times 10^{-6}}{RC}$$

$$RC \ln 2 = 10 \times 10^{-6} \implies \boxed{RC = 14.427 \,\mu\text{s}}$$

If the capacitor is set at **0.01 micro-Farads**, then it follows that the resistor must be **1442.7 ohms**.

Square Wave Calculations

Assuming a capacitor is "fully charged" at $t=5\tau$ and that the square wave's period includes both a positive and negative section:

$$t = 5 \times 14.427 \,\mu\text{s} = 72.135 \,\mu\text{s}$$

$$T = 2 \times 72.135 \,\mu\text{s} = 144.27 \,\mu\text{s}$$

$$f = \frac{1}{T} \implies \boxed{f = 6.931 \,\mathrm{kHz}}$$

Results

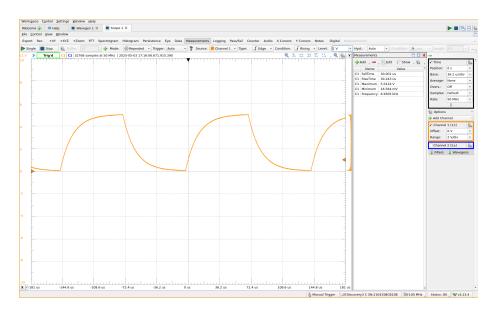


Figure 1: Oscilloscope View

Conclusion (Ceramic vs Electrolytic Capacitors)

Ceramic capacitors use ceramic as the dielectric between the conducting plates whereas electrolytic capacitors use a thin oxide layer on metal as the dielectric. The polarity determines which way the voltage drop/gain across a capacitor must face. For ceramic capacitors, this direction doesn't matter, and so they are said to be non-polarized. Electrolytic capacitors, on the other hand, do have a

polarity, and need to be placed in a circuit where the positive and negative (or smaller voltage) nodes match the capacitor.