

# Lab 6 Thevenin Equivalent

Jonah Spector — Lab Section: 001

2025-03-29

## Introduction

Thevenin equivalence is a powerful tool for analyzing the properties of more complex circuits. It allows engineers to understand the power output a single part of a circuit while ignoring the internal components. This can be used to understand amplifiers, power supplies, and maximally efficient electric lighting circuits, for example.

## Exercise I

Bridge circuit data:

$R_{\text{load}}$ ( $\Omega$ )	$I_{\text{load}}$ (mA)	$V_{ab}$ (V)
Inf.	0	4.11
47k	0.08	3.959
20k	0.19	3.766
10k	0.35	3.476
4.7k	0.63	2.962
2.2k	1.03	2.241
1k	1.47	1.456
470	1.81	0.845
100	2.16	0.214
0	2.28	0

```
from math import *

import numpy as np
import matplotlib.pyplot as plt

exercise_1 = np.array([
    [np.inf, 0, 4.11],
    [47000, 0.08, 3.959],
```

```

        [20000, 0.19, 3.766],
        [10000, 0.35, 3.476],
        [4700, 0.63, 2.962],
        [2200, 1.03, 2.241],
        [1000, 1.47, 1.456],
        [470, 1.81, 0.845],
        [100, 2.16, 0.214],
        [0, 2.28, 0],
    ])

z = np.polyfit(exercise_1[:,1], exercise_1[:,2], 1)
p = np.poly1d(z)

plt.plot(exercise_1[:,1], p(exercise_1[:,1]))
plt.scatter(exercise_1[:,1], exercise_1[:,2])
plt.title("Bridge Circuit")
plt.xlabel("Current [mA]")
plt.ylabel("Voltage [V]")
plt.grid()

print(f"The curve is linear. The slope is: {z[1]} V/mA")
print(f"{z[1]*1000} V/A (ohm)")

```

The curve is linear. The slope is: 4.104488722955604 V/mA  
4104.488722955603 V/A (ohm)

The short circuit resistance between (a) and (b) was around 2.5 k ohm when measured. This is a seemingly unusual reading which doesn't match the slope or the Thevenin resistance. It could be caused by an issue with the waveform generator adding resistance to the circuit since it remained attached but off.

With the Thevenin voltage (open circuit voltage) and Norton current (short circuit current), the Thevenin equivalent circuit can be made.

$$V_{th} = 4.11 \text{ V} \quad I_N = 2.28 \text{ mA}$$

$$R_{th} = \frac{V_{th}}{I_N} = 1802.63 \, \Omega$$

Thevenin equivalent circuit data (using a 2.2 k ohm resistor to approximate the  $R_{th}$  of 1.803 k ohm):

$R_{load} \, (\Omega)$	$I_{load} \, (\text{mA})$	$V_{ab} \, (\text{V})$
Inf.	0	4

$R_{\text{load}}$ ( $\Omega$ )	$I_{\text{load}}$ (mA)	$V_{ab}$ (V)
47k	0.08	3.926
20k	0.18	3.702
10k	0.33	3.368
4.7k	0.59	2.799
2.2k	0.93	2.055
1k	1.28	1.284
470	1.54	0.724
100	1.79	0.178
0	2	0

```

from math import *

import numpy as np
import matplotlib.pyplot as plt

exercise_1b = np.array([
    [np.inf, 0, 4.100],
    [47000, 0.08, 3.926],
    [20000, 0.18, 3.702],
    [10000, 0.33, 3.368],
    [4700, 0.59, 2.799],
    [2200, 0.93, 2.055],
    [1000, 1.28, 1.284],
    [470, 1.54, 0.724],
    [100, 1.79, 0.178],
    [0, 1.88, 0],
])

zb = np.polyfit(exercise_1b[:,1], exercise_1b[:,2], 1)
pb = np.poly1d(zb)

plt.plot(exercise_1b[:,1], pb(exercise_1b[:,1]))
plt.scatter(exercise_1b[:,1], exercise_1b[:,2])
plt.title("Thevenin Circuit")
plt.xlabel("Current [mA]")
plt.ylabel("Voltage [V]")
plt.grid()

print(f"The curve is linear. The slope is: {zb[1]} V/mA")
print(f"{zb[1]*1000} V/A (ohm)")

The curve is linear. The slope is: 4.093991496223372 V/mA
4093.9914962233715 V/A (ohm)

```

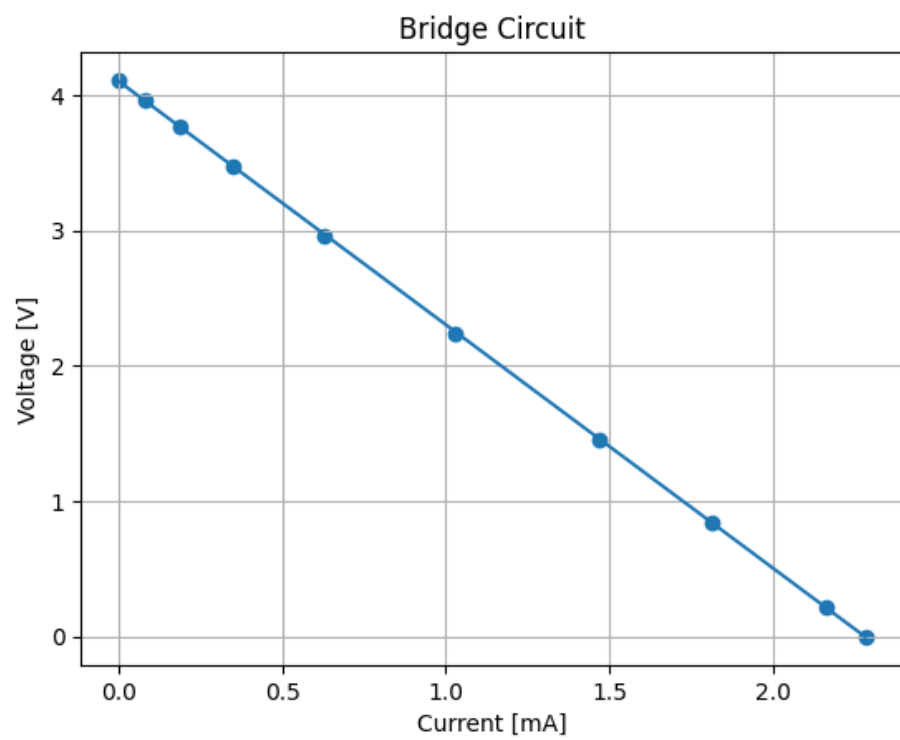


Figure 1: Bridge Graph

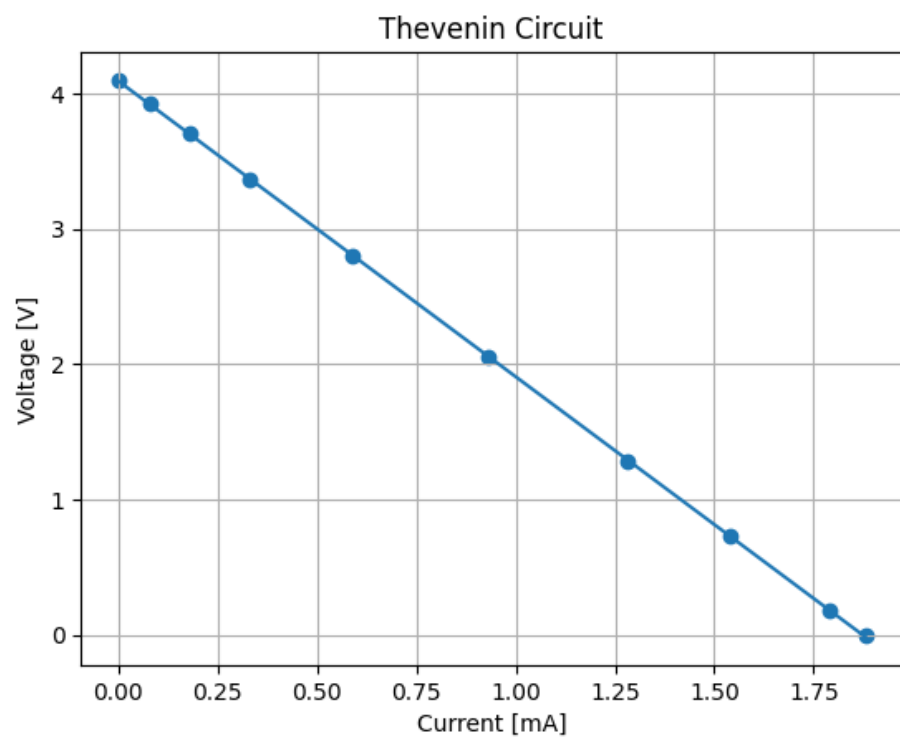


Figure 2: Thevenin Graph

Both graphs together:

```
plt.plot(exercise_1[:,1], p(exercise_1[:,1]))
plt.scatter(exercise_1[:,1], exercise_1[:,2])
plt.plot(exercise_1b[:,1], pb(exercise_1b[:,1]))
plt.scatter(exercise_1b[:,1], exercise_1b[:,2])
plt.title("Thevenin vs Bridge Circuit")
plt.xlabel("Current [mA]")
plt.ylabel("Voltage [V]")
plt.grid()
plt.legend(["Bridge", "Bridge Data", "Thevenin", "Thevenin Data"])
```

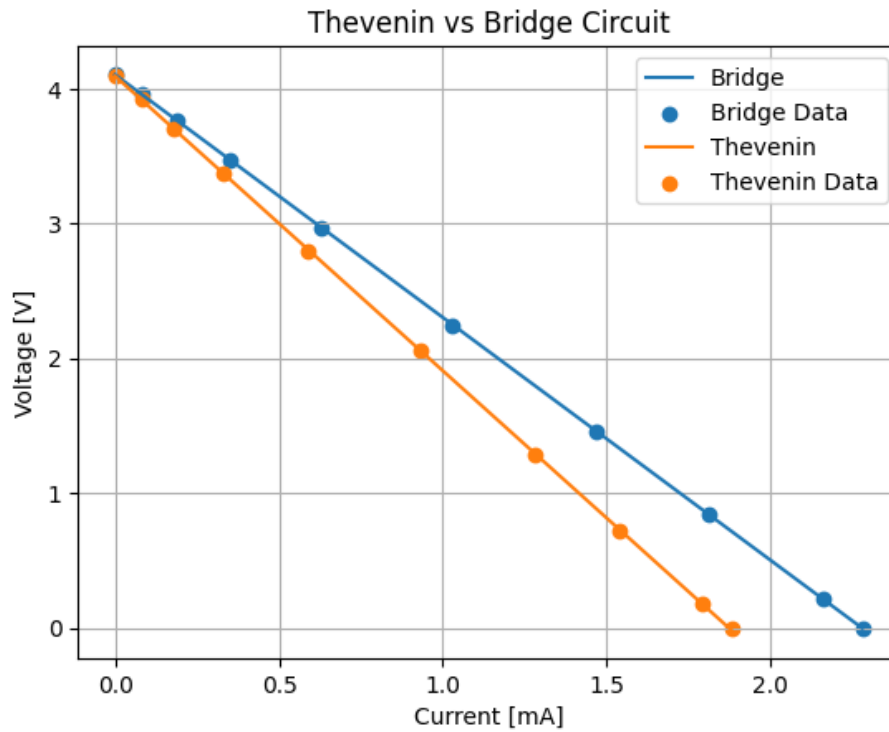


Figure 3: Graph of Both

The difference is almost entirely due to the different  $R_{th}$  resistors used. If a resistor closer to 1.803 k ohm instead of 2.2 k ohm was chosen, the lines would be much closer to each other. Besides that, they are quite similar, which shows the principle of Thevenin equivalence.

## Exercise II

Calculated using  $P = VI$  and a calculator, no Python.

$R_{\text{load}} (\Omega)$	$P_L (\text{mW})$
Inf.	0
47k	0.314
20k	0.666
10k	1.111
4.7k	1.651
2.2k	1.911
1k	1.644
470	1.115
100	0.319
0	0

The maximum power transfer is given by:

$$R_L = R_{th} \implies$$

$$P_{\max} = \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 R_L = \left( \frac{V_{th}}{2R_{th}} \right)^2 R_{th}$$

```
r_l = np.array([47000, 20000, 10000, 4700, 2200, 1000, 470, 100, 0])
p_l = np.array([0.314, 0.666, 1.111, 1.651, 1.911, 1.644, 1.115, 0.319, 0])
```

```
r = np.linspace(0, 47000, 10000)
```

```
# Using 2.2 k ohm for the R_th here to match actual circuit values
```

```
plt.plot(r/1000, (r*(4.1/(2200 + r))*2)*1000)
plt.plot(r/1000, r*0 + 1000*2200*(4.1/(2*2200))*2)
plt.scatter(r_l/1000, p_l)
plt.title("Power Transfer")
plt.xlabel("Resistance [k ohm]")
plt.ylabel("Power [mW]")
plt.grid()
plt.legend(["Power Transfer", "Theoretical Max Power", "Data"])
```

The 2.2 k ohm maximizes the power in the graph, which makes sense since it is the same as the Thevenin resistance. It is the asymptote of the graph for  $R_L$  approaches infinity is 0, which makes sense since infinite resistance blocks all current and power is  $P = VI$ . To check each resistor's power output to verify one maximizes the output, you could let each resistor reach equilibrium temperature

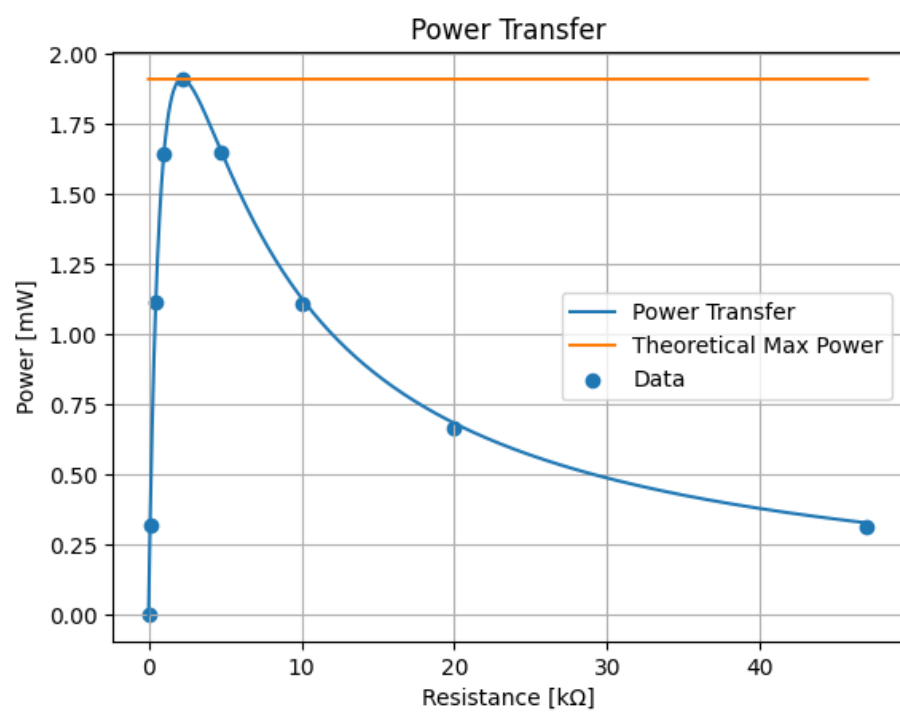


Figure 4: Power Graph



and find whichever resistor produces the most heat (is at the highest equilibrium temperature).

## Conclusion

Throughout this lab, the principles of Thevenin equivalence and the methods to calculate it, including Norton current, were utilized extensively. The equations all matched with reality to some degree, with only a small discrepancy for  $R_{th}$  and the different value chosen for the physical Thevenin circuit.