

Lab 5: Series and Parallel Resistors

Jonah Spector — Lab Section: 001

2025-03-02

Introduction

Kirchhoff's Current and Voltage Laws are essential for circuit analysis. Understanding their applications and method of calculation through real world circuits helps to ground their concepts in reality.

Exercise A

- 1) The multimeter reads the current from (b) to (c') and the voltage between (b) and (c'), and (a) and (c').

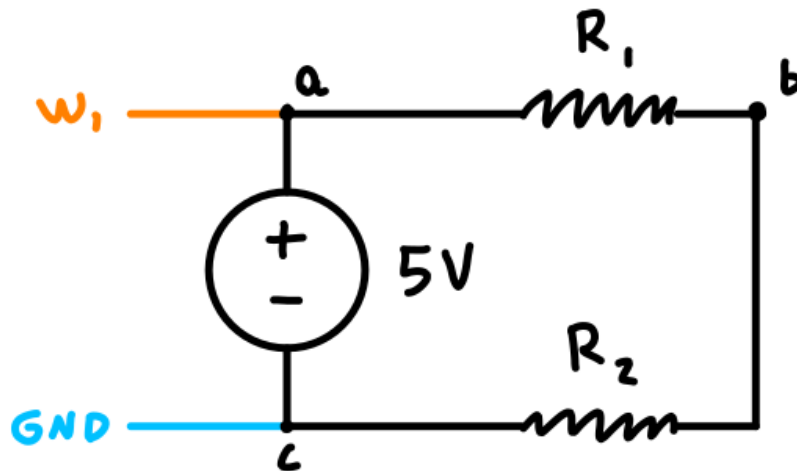


Figure 1: Voltage Divider

- 2) Assuming V_{out} is the voltage after R_1 /across R_2 , between node (b) and (c'), to find the values of R_1 and R_2 given a required V_{out} and required I ,

with arbitrary V :

$$V_{out} = IR_2 \Rightarrow \boxed{R_2 = \frac{V_{out}}{I}}$$

$$V = IR_1 + V_{out} \Rightarrow \boxed{R_1 = \frac{V - V_{out}}{I}}$$

With $V = 5\text{V}$, $V_{out} = 0.05\text{V}$ and $I = 5\text{mA}$, $\boxed{R_1 = 990\Omega}$ and $\boxed{R_2 = 10\Omega}$

- 3) $V_{out} = 52.1\text{mV}$ and $I_T = 5.1\text{mA}$.
- 4) The measurements are very close to the predicted values, but any difference can be explained by the resistance in the wires or resistor accuracy being off.

Exercise B

- 1) The multimeter reads the current across R_1 , R_2 , and the total current, and the voltage between (a) and (b).

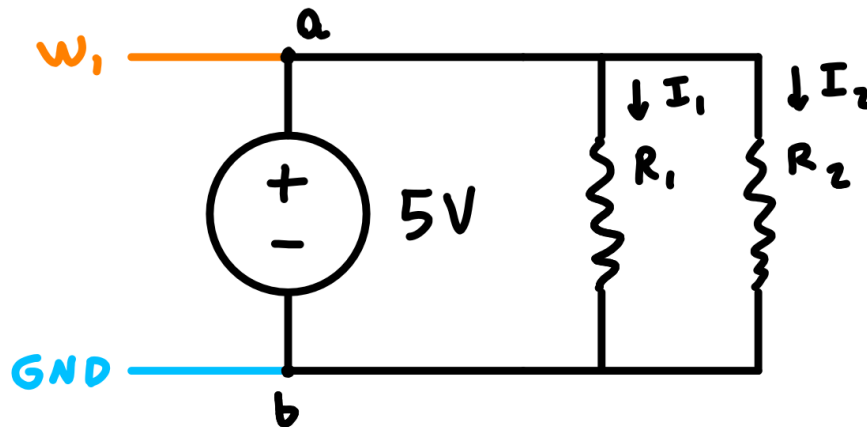


Figure 2: Current Divider

- 2) Given the constraints:

$$I_1 + I_2 = 3I_2 + I_2 = 4I_2 = I_T$$

$$V = R_2 I_2 = R_2 \frac{I_T}{4}$$

$$R_2 = \frac{4V}{I_T}$$

$$V = R_1 I_1 = R_1 \frac{3I_T}{4}$$

$$R_1 = \frac{4V}{3I_T}$$

With $I_T = 5\text{mA}$ and $V = 5\text{V}$:

$$R_1 = 1333\Omega$$

$$R_2 = 4000\Omega$$

- 3) $I_1 = 3.80\text{mA}$, $I_2 = 1.22\text{mA}$, and $I_T = 5.1\text{mA}$.
- 4) The measurements were significantly closer to the theoretical values than exercise A. The discrepancy could again have come from the resistor thresholds and multimeter inaccuracy.

Exercise C

1)	V_s	I_1	I_2
5V	2.3 mA	1.0 mA	1.3 mA
-5V	-2.3 mA	-1.0 mA	-1.3 mA

- 2) Yes. The current into the node equals the current out, and the measured values were almost perfectly demonstrative of this.

Exercise D

- 1) Assuming the voltages across each branch are for each resistor 1-3, the multimeter measured values are:

$$V_1 = 4.99\text{V}, V_2 = 7.2\text{V}, V_3 = 2.8\text{V}$$

2) All three resistors have negative polarities for their respective loops following the passive sign convention.

3)

$$0 = 5 - 4.99$$

4)

$$0 = -(4.99) + 7.8 - (2.8)$$

5) Yes, with acceptable measurement error.

Exercise E

1)

	1	2	3	4
V	-1.760 V	-0.680 V	0.681 V	-2.607 V
I	-2.8 mA	-2.03 mA	2.3 mA	2.7 mA

2) Combining the resistors in parallel, then three in series and using Ohms' Law: 2.7 mA.

3)

	1	2	3	4
P	4.7 mW	1.4 mW	1.5 mW	-7.0 mW

4) Sum of powers: 0.6 mW

Conclusion

Both of Kirchhoff's Laws were proven to work for actual circuits. The values gathered throughout this lab were in line with both laws for the most part, with small discrepancies likely coming from resistor thresholds and multimeter error.